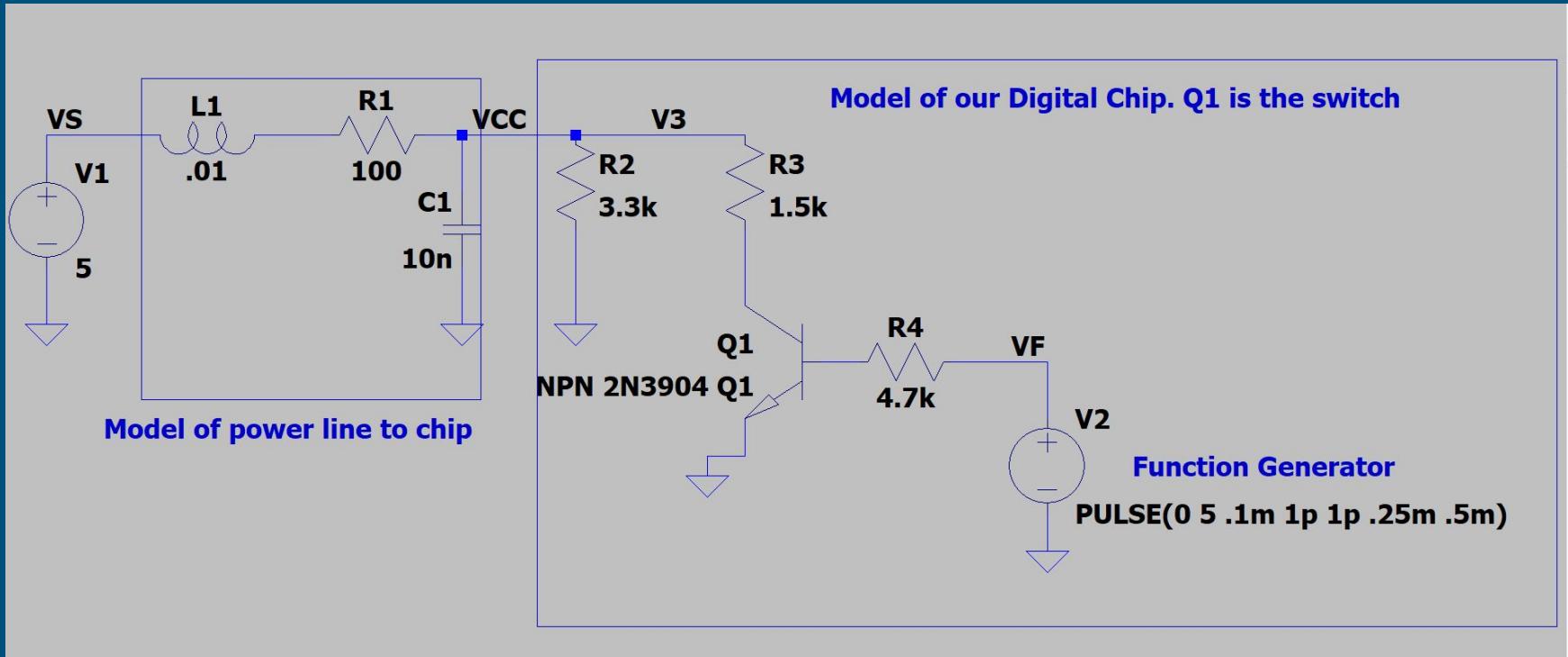




Surge Suppressor Project Group 1

Madison Klementyn, Jasmine Koski,
Risto Rushford
July 22, 2020


Original Circuit



Noisy Circuit

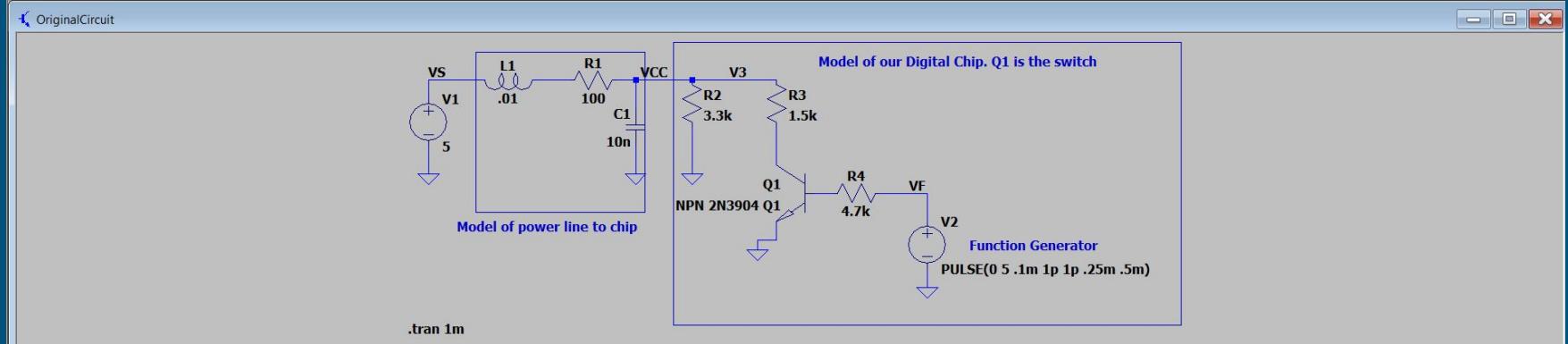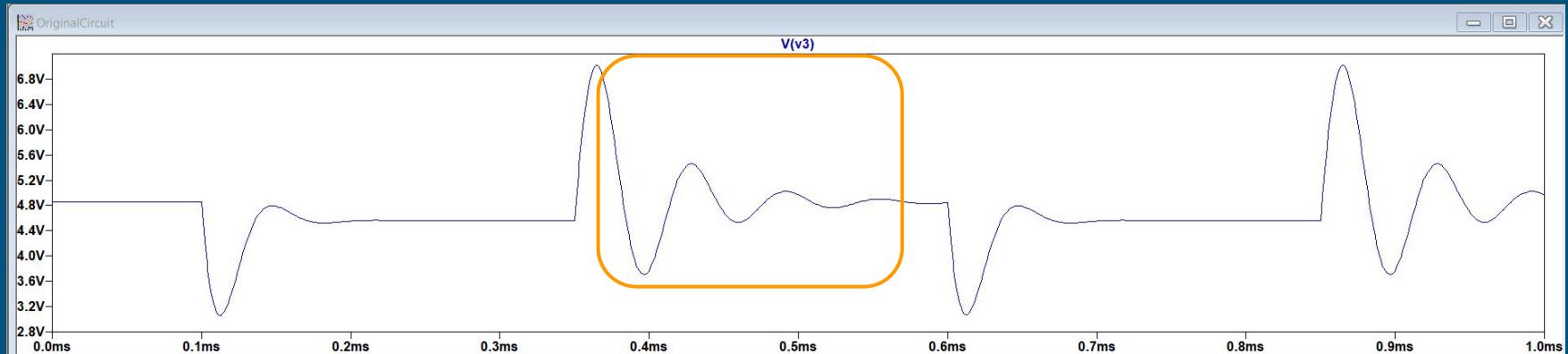

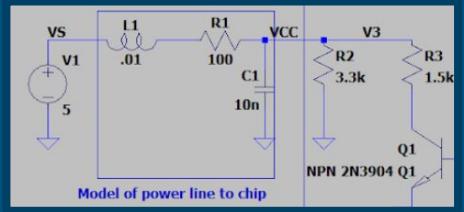Hand Calculations - Original Circuit Transfer Function H(s)



$$\frac{\left(\frac{1}{sC} \right)}{sL + R1 + \left(\frac{1}{sC} \right)}$$

Hand Calculations - Original Circuit Transfer Function H(s)

$$H(s) = \left. \frac{\frac{1}{s10E-9}}{\frac{1}{s10E-9} + s0.10 + 100} \right|_s$$


$$H(j\omega) = \left. \frac{\frac{1}{j\omega10E-9}}{\frac{1}{j\omega10E-9} + j\omega0.10 + 100} \right|_{s=(j\omega)}$$

$$\omega = 2\pi f$$

$$\omega = 2\pi 2kHz$$

$$\omega = 12566 \frac{rad}{s}$$

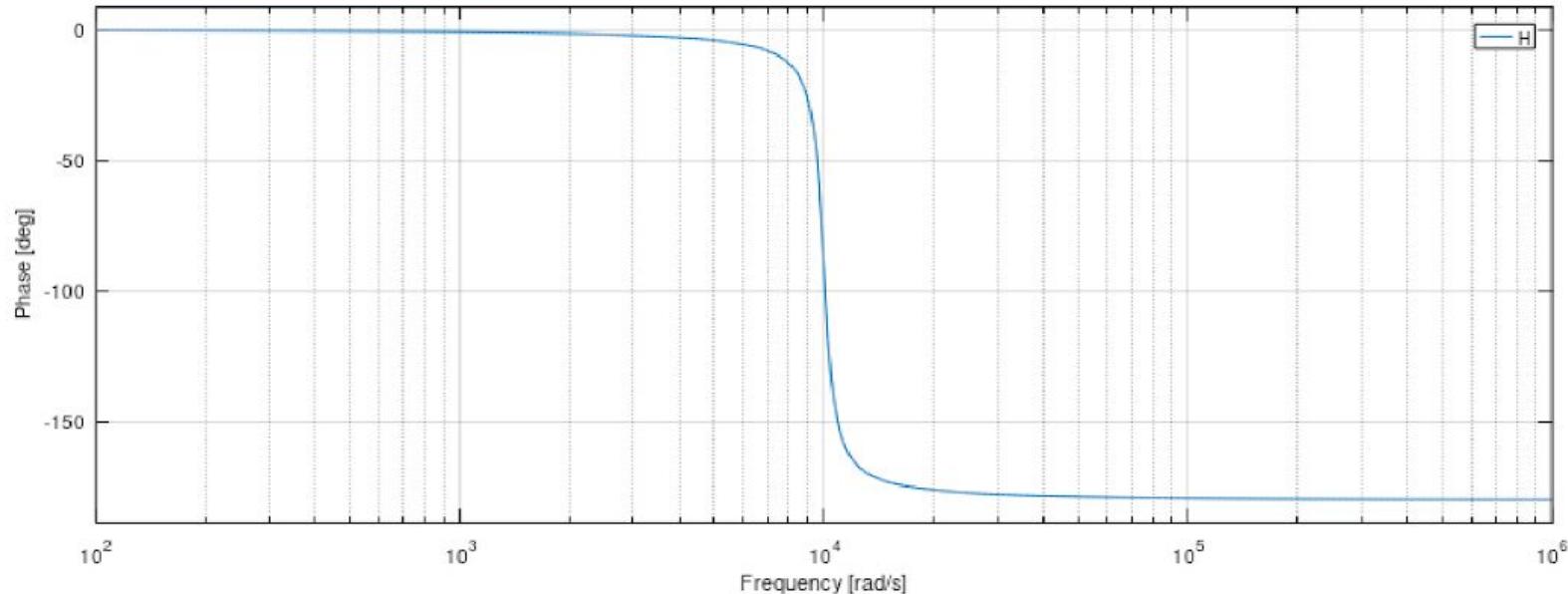Hand Calculations - Original Circuit Bode & Phase Plots



Hand Calculations - Original Circuit Transfer Function H(s)

$$H(j12566) = \frac{\frac{1}{j12566 \cdot 10E-9}}{\frac{1}{(j12566) \cdot 10E-9} + (j12566 \cdot 0.10) + 100} \Big|_{s=(j12566)}$$

$$H(j12566) = 1.184019 - j17.71648$$

$$H(j12566) = 1.18 \angle -0.855^\circ$$



Hand Calculations - Original Circuit


Vout

$$v_o(t) = A|H(j\omega)| \cos(\omega t - \theta(\omega))$$

$$v_o(t) = (5)|(1.18)| \cos(12566t - (-0.855^\circ))$$

$$v_o(t) = 5.9 \cdot \cos(12566t + 0.855^\circ) V$$

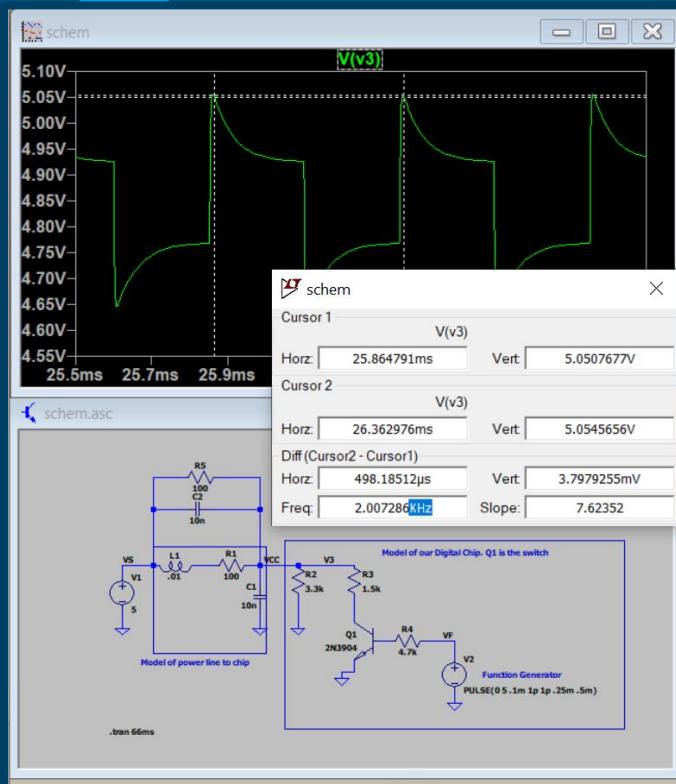Hand Calculations - “The Fix” Transfer Function H(s)



$$\frac{\left(\frac{1}{\left(s10E - 9 + \frac{1}{3300} + \frac{1}{1500} \right)} \right)}{\left(\frac{1}{\left(s10E - 9 + \frac{1}{3300} + \frac{1}{1500} \right)} \right) + \left(\frac{1}{s10E - 9 + \left(\frac{1}{100} \right) + \left(\frac{1}{s0.10 + 100} \right)} \right)}$$

<https://rb.gy/miyhyh>

$$\omega = 2\pi f$$

$$\omega = 2\pi 2kHz$$

$$\omega = 12566 \frac{rad}{s}$$

Hand Calculations - “The Fix” Transfer Function H(s)

$$= \frac{0.00000001s + \frac{0.1s + 200}{10s + 10000}}{0.00000001s + \frac{1.0E - 15s^3 + 1.09797E - 9s^2 + 2.09697E - 6s + \frac{0.0000000001s^3 + 0.0001s^2 + 0.42929s + 419.39393}{0.1s + 100}}{0.00000001s^2 + 0.0001s + \frac{0.01s^2 + 30s + 20000}{0.1s + 100}}}$$



Hand Calculations - “The Fix” Transfer Function H(s)

$$H(s) = \frac{\left(\frac{1}{(s10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right)}{\left(\frac{1}{(s10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right) + \left(\frac{1}{s10E-9 + (\frac{1}{100}) + (\frac{1}{s0.10+100})} \right)}$$

$$H(j\omega) = \frac{\left(\frac{1}{((j\omega)10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right)}{\left(\frac{1}{((j\omega)10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right) + \left(\frac{1}{(j\omega)10E-9 + (\frac{1}{100}) + (\frac{1}{(j\omega)0.10+100})} \right)} \Bigg|_{s=(j\omega)}$$

Hand Calculations - “The Fix” Transfer Function H(s)

$$H(j12566) = \frac{\left(\frac{1}{((j12566)10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right)}{\left(\frac{1}{((j12566)10E-9 + \frac{1}{3300} + \frac{1}{1500})} \right) + \left(\frac{1}{(j12566)10E-9 + \left(\frac{1}{100}\right) + \left(\frac{1}{(j12566)0.10+100}\right)} \right)} \Bigg|_{s=(j12566)}$$

$$H(j12566) = 0.91287 - j0.01565$$

$$H(j12566) = 0.9130 \angle -0.982^\circ$$

Hand Calculations - “The Fix”



Vout

$$v_o(t) = A|H(j\omega)|\cos(\omega t - \theta(\omega))$$



$$v_o(t) = (5)|(0.9130)|\cos(12566t - (-0.982^\circ))$$

$$v_o(t) = 4.565 \cdot \cos(12566t + 0.982^\circ)V$$



Noise in Original Circuit

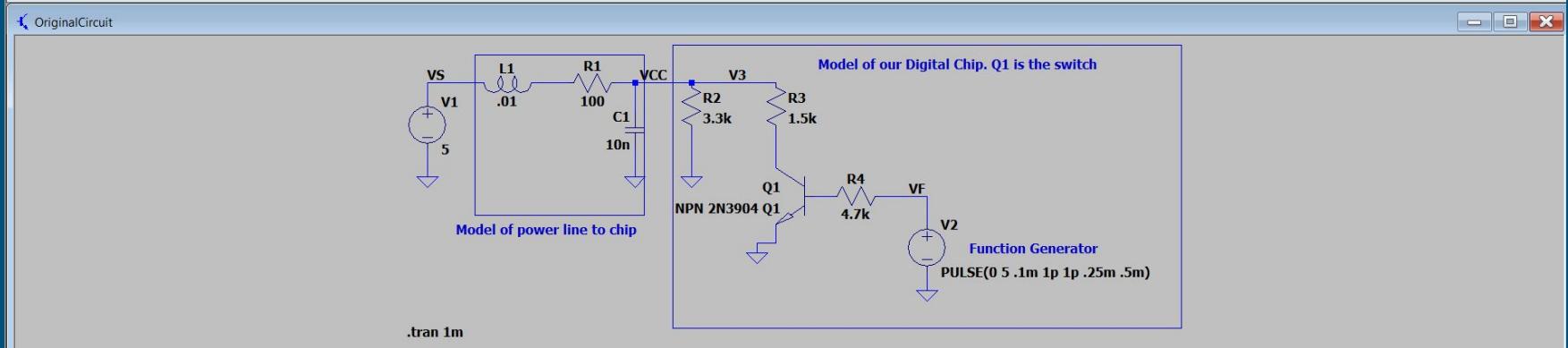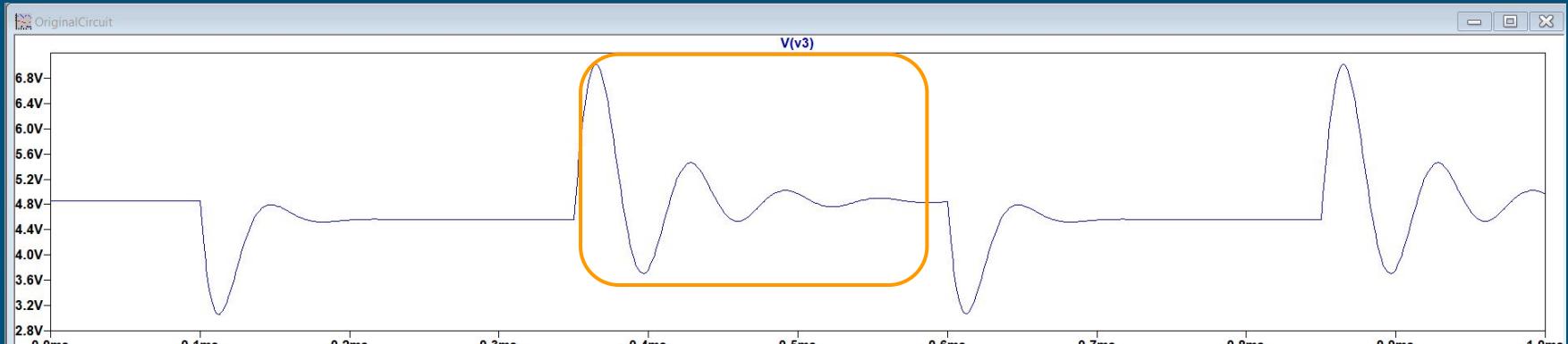


Series RC Circuit Added

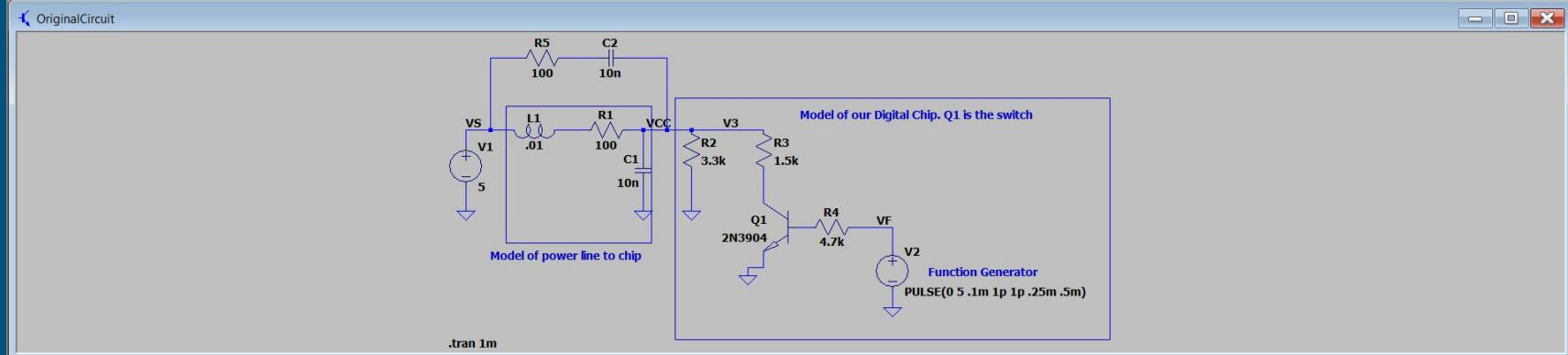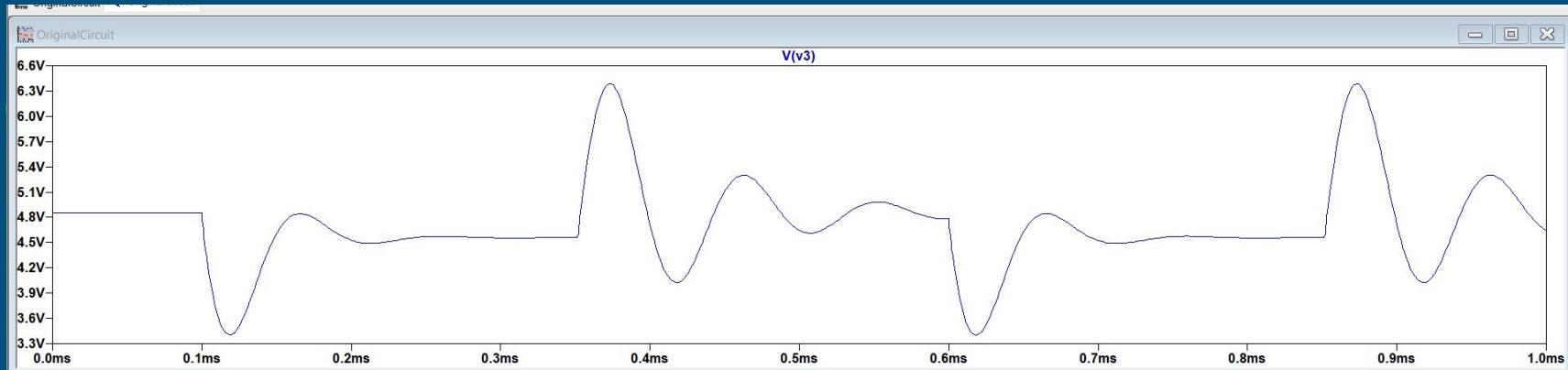



Series RC Circuit Added

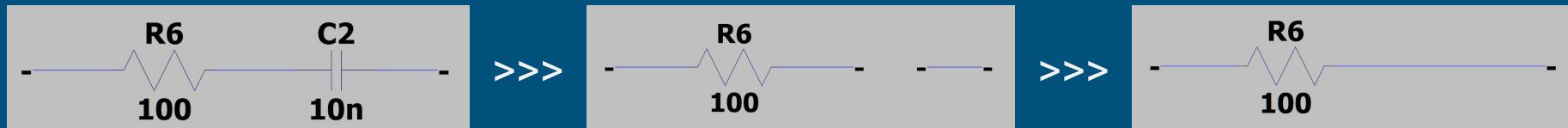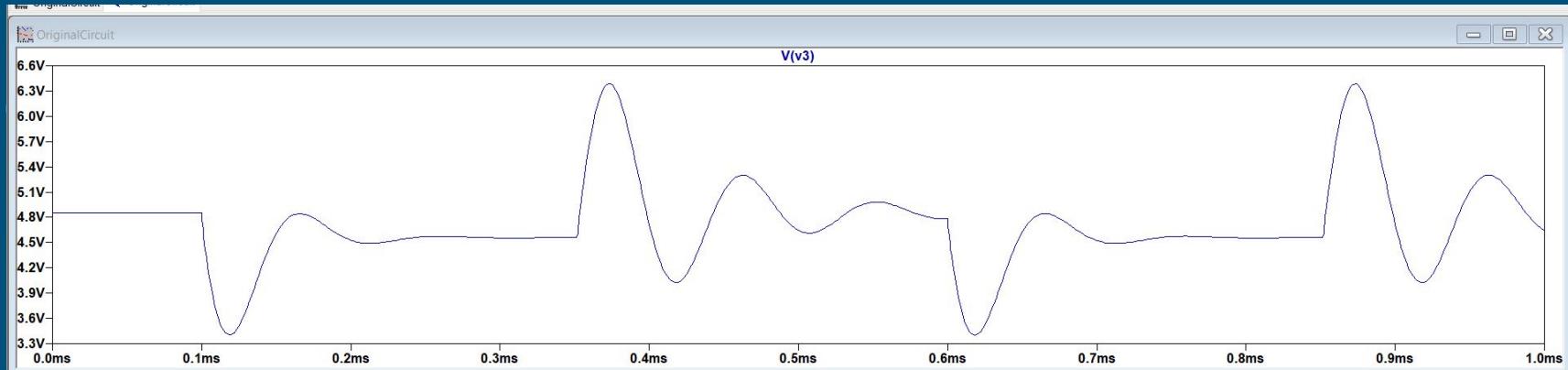



First Parallel RC Circuit Added

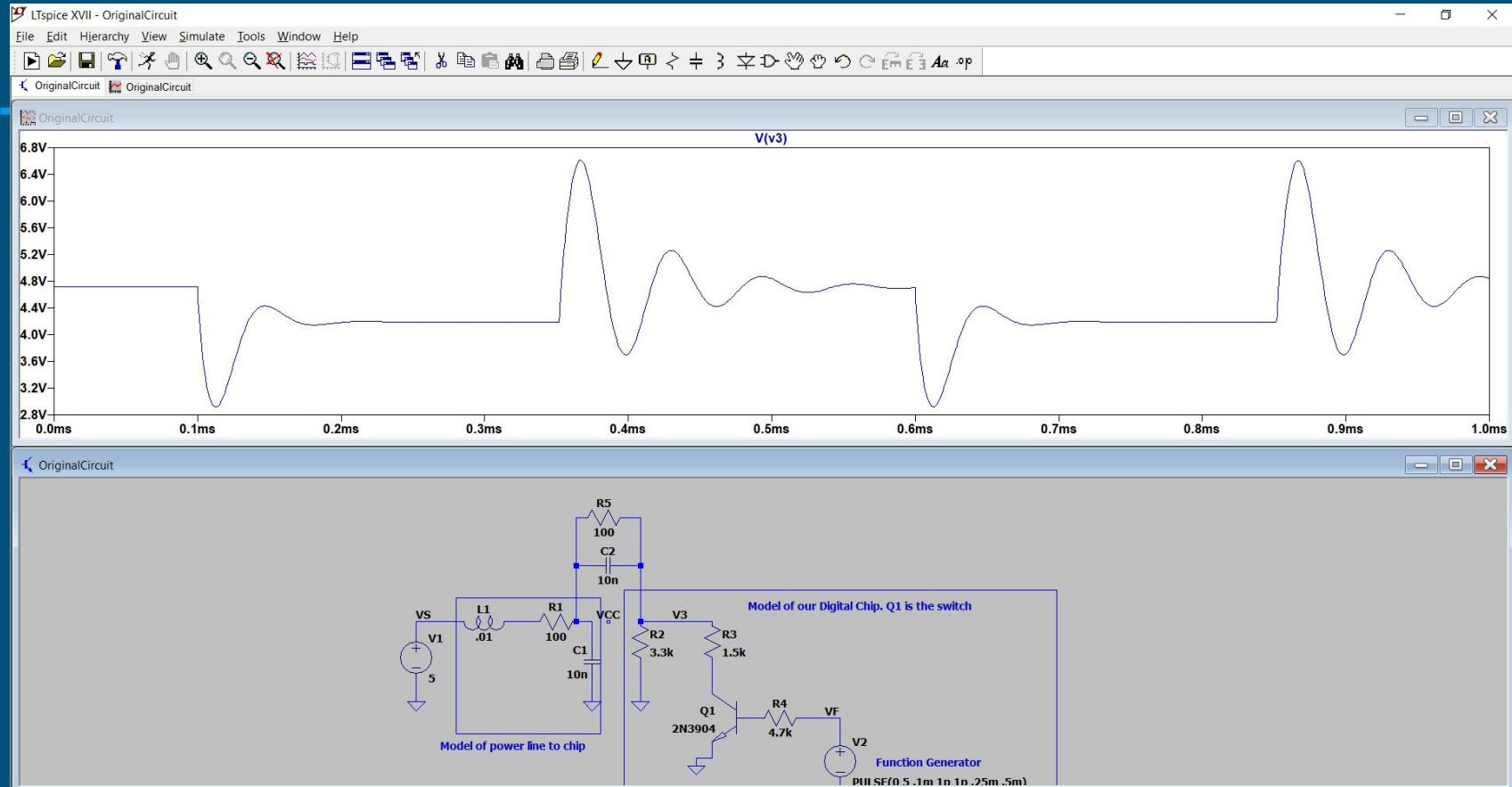


Better Parallel RC Circuit Added

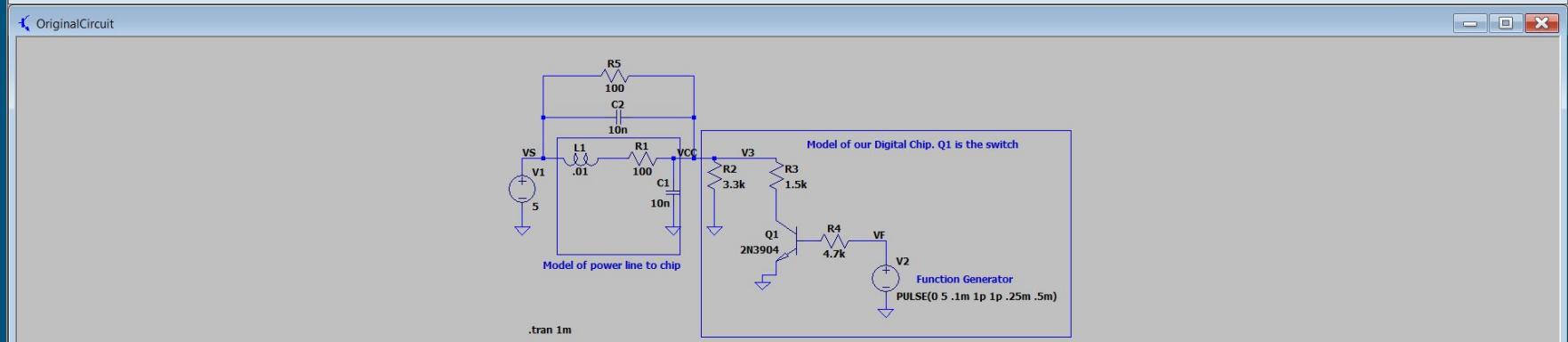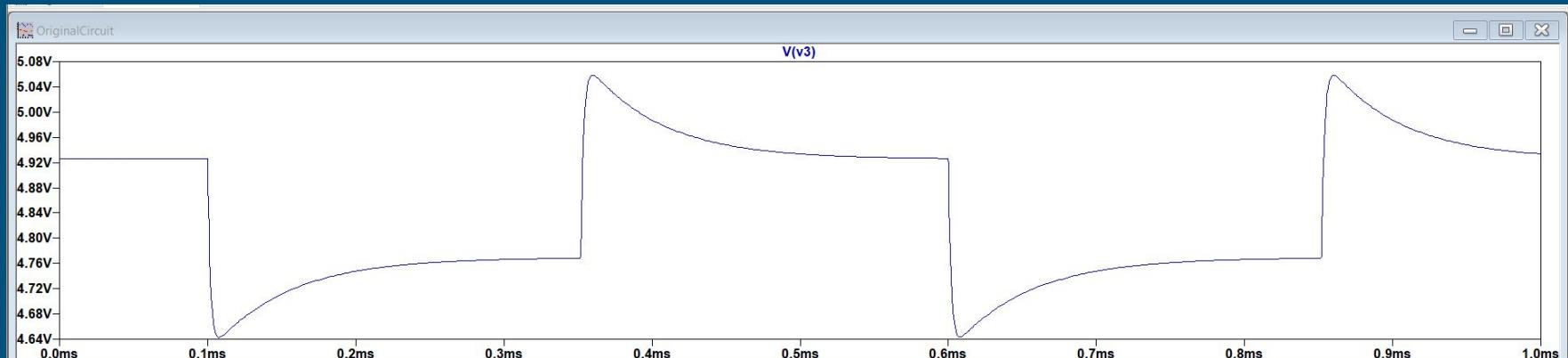


Better Parallel RC Circuit Added

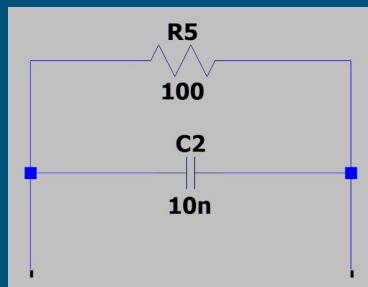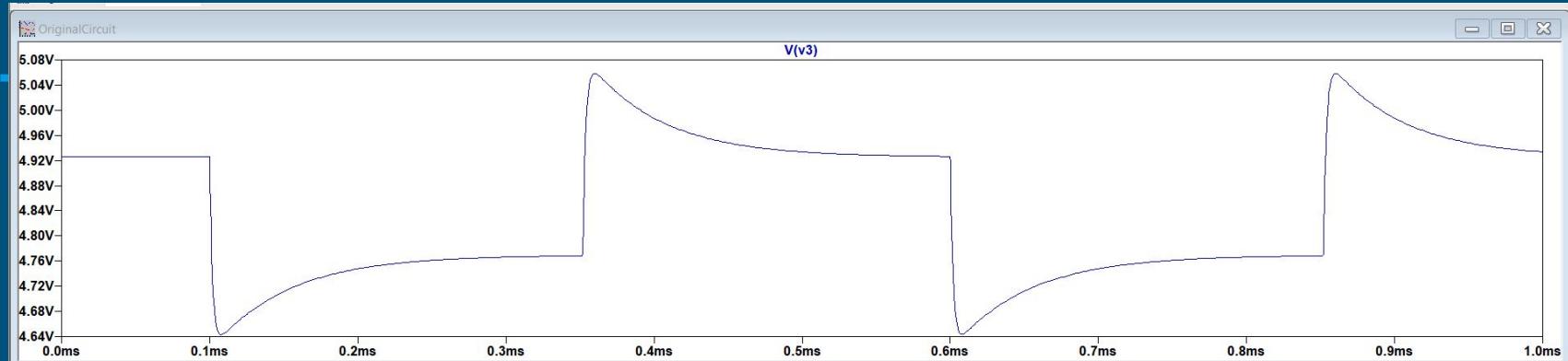


>>>

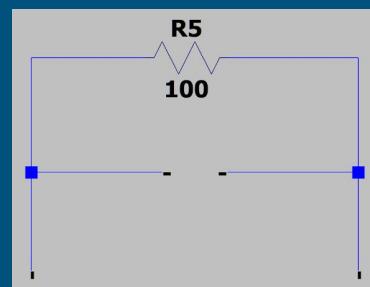

>>>

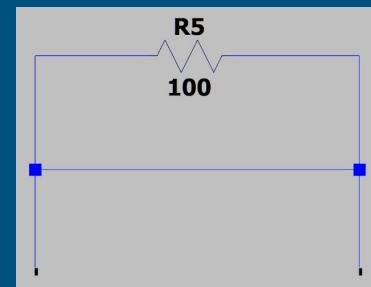

Results Close To 100 Ohm Resistor Alone

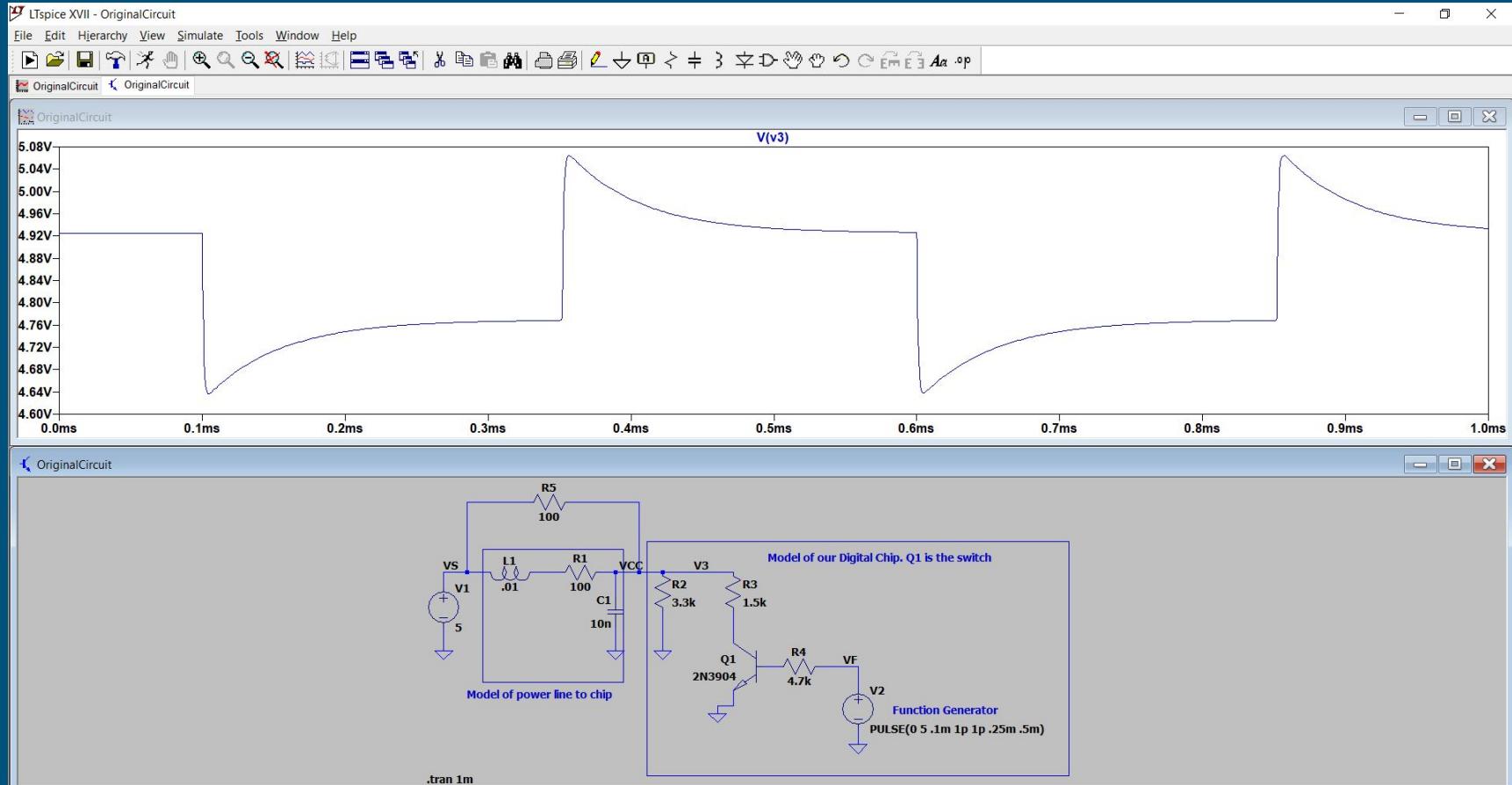


RC vs. RL Circuit Noise

An inductor introduces more noise to the circuit than a capacitor.


Placing components in parallel is more effective for noise reduction than placing them in series.



Physical Circuit without Filter

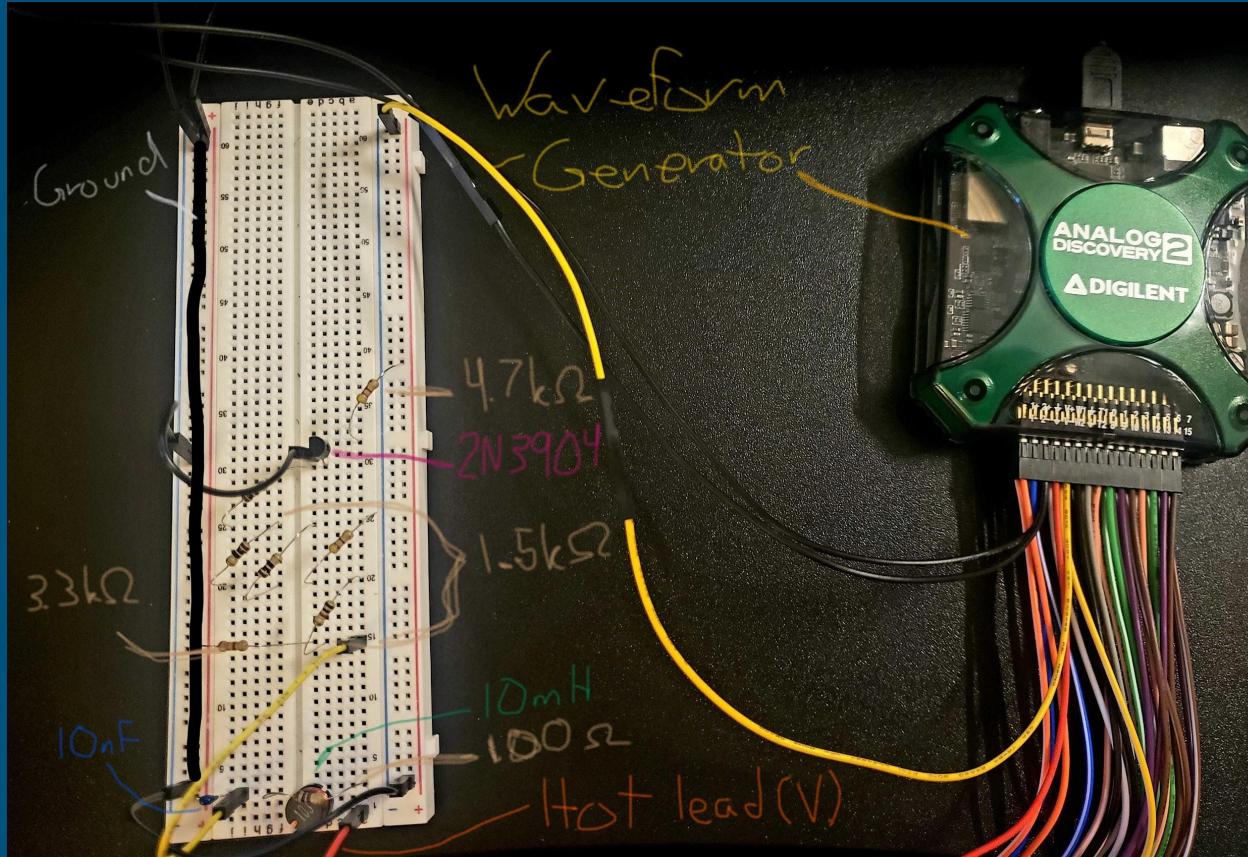


Physical Circuit without Filter

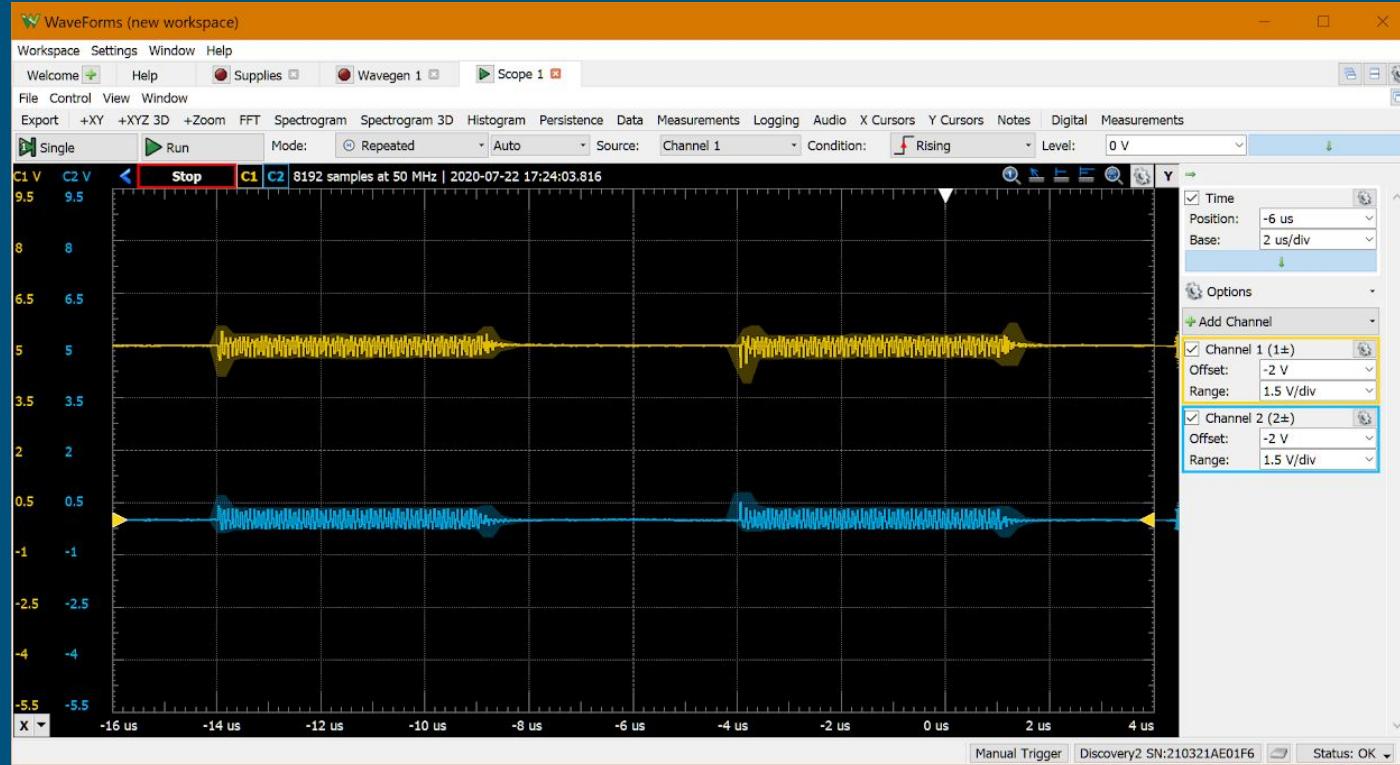


Note: we haven't gotten to fully troubleshoot the waveform generator and make sure we had the correct set-up. Will improve for next project if able to.

Physical Circuit with Filter

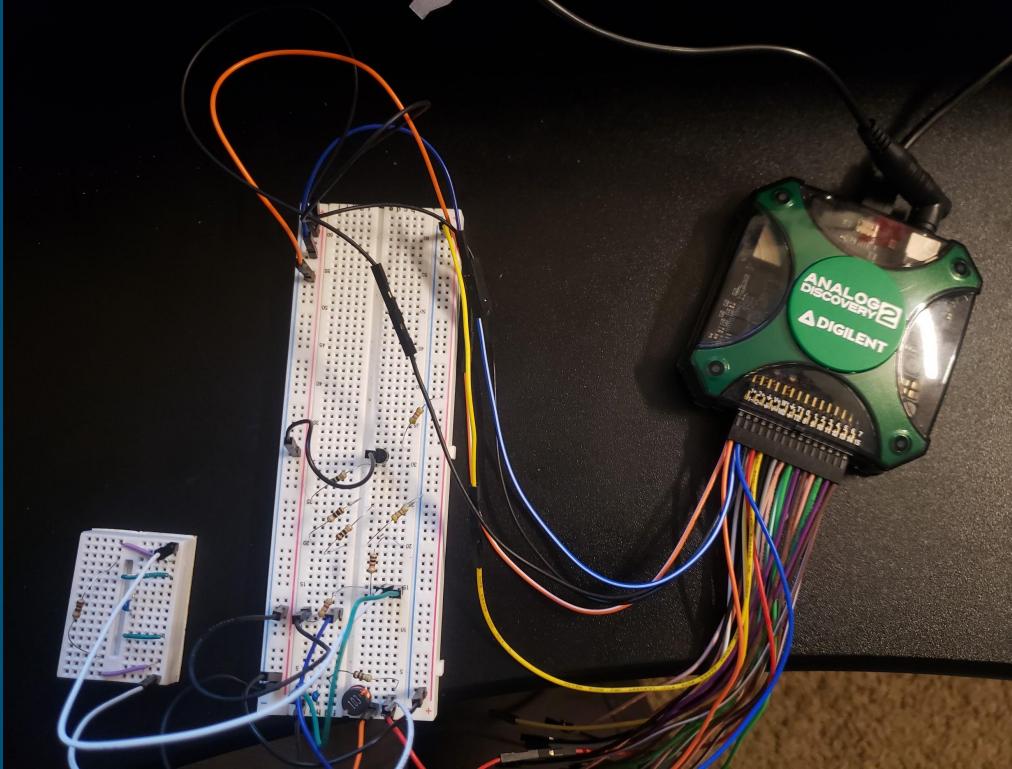

Note: Relating to issue on previous slide, no analysis of circuit with filter.

Conclusion: Best Noise Reduction Circuit

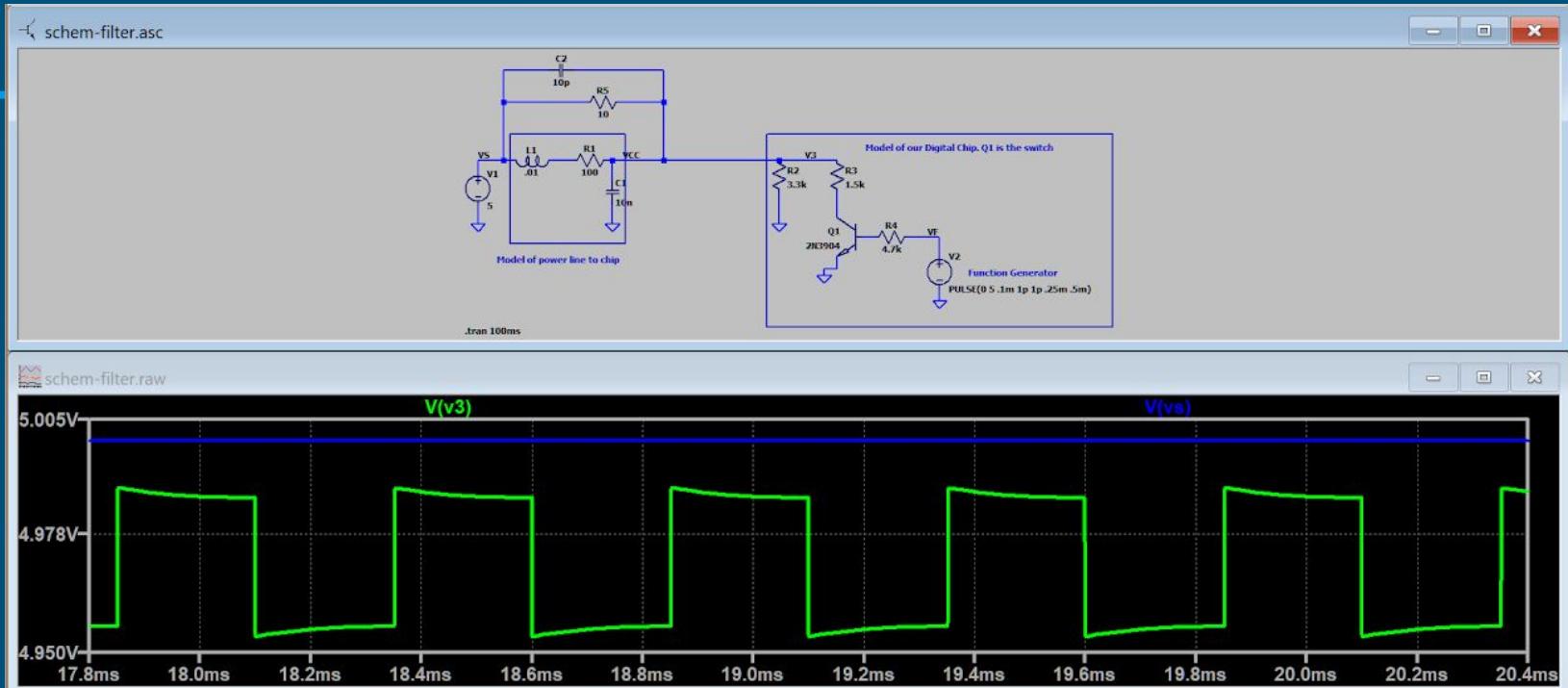

Best Components from Appendix H: 10 pF capacitor in parallel to 10 Ω resistor

Questions?
